

ASM Design II

Harry Beadle

To design more generic systems we need to be able to utilise inputs. Inputs are shown as decision diamonds in ASM charts.

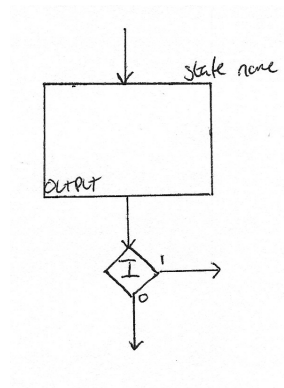


Figure 1: An input in a ASM chart.

Now we can use inputs let's design a 2-bit counter that counts up and down based on an input. The input, **MODE** or **M**, will cause the counter to count up when it is '0' and count down when it is '1'.

To make it slightly easier we will use grey coding. This is a binary system where only one bit changes per increment.

Denary	Binary	Grey Encoding
0	00	00
1	01	01
2	10	11
3	11	10

First we design an ASM chart.

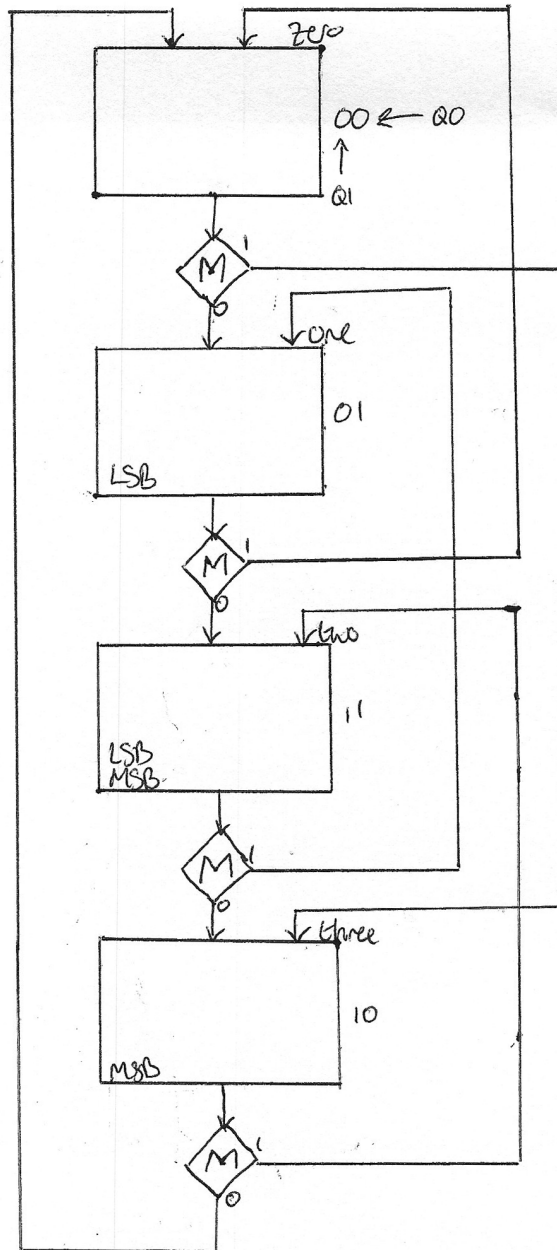


Figure 2: The ASM Chart

Then we allocate state variables, which are shown on the ASM chart. Next we

form a State Transition Table.

M	$Q1$	$Q0$	$Q1_n$	$Q0_n$	MSB	LSB
0	0	0	0	1	0	0
0	0	1	1	1	0	1
0	1	0	0	0	1	0
0	1	1	1	0	1	1
1	0	0	1	0	0	0
1	0	1	0	0	0	1
1	1	0	1	1	1	0
1	1	1	0	1	1	1

Next we can for equations for the next state.

$$Q1_n = \overline{M}Q0 + M\overline{Q0}$$

$$Q0_n = \overline{M} \overline{Q1} + MQ1$$

$$MSB = Q1; \quad LSB = Q0$$

Then finally this can be implemented in hardware, using a slightly new technique to keep things cleaner when in larger systems.

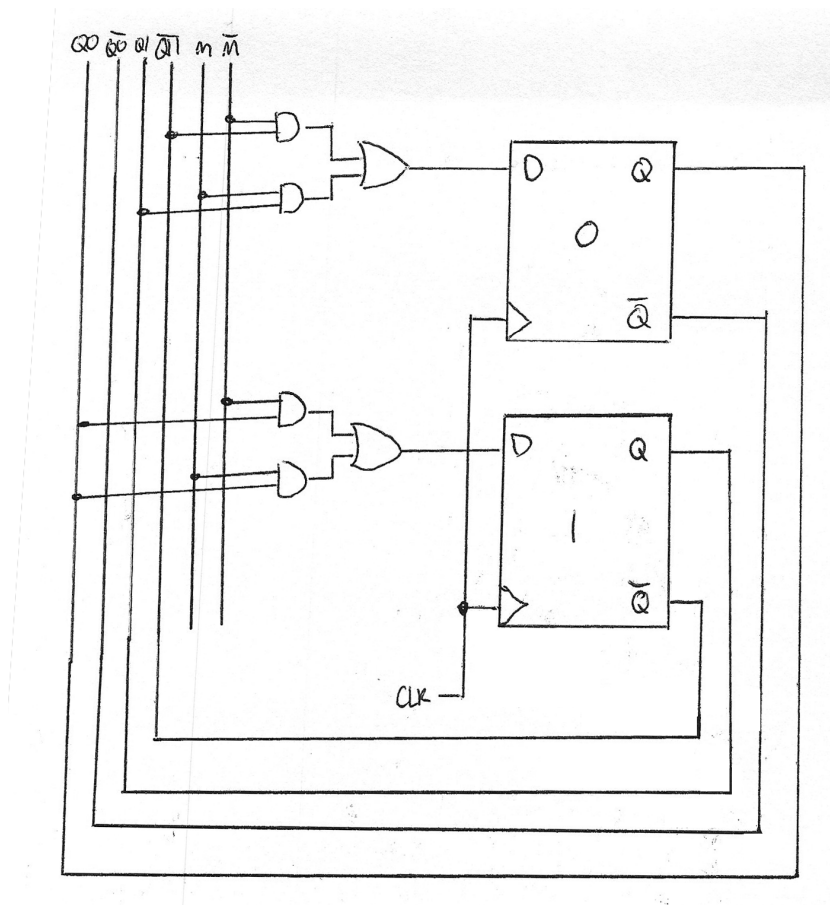


Figure 3: The circuit diagram for the counter.